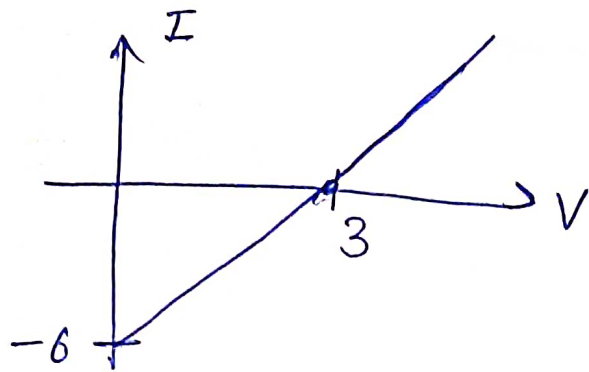


Q1



Quiz-2

Diksha Sethi

2020056

Sec A

ECE13

Basic Elec

When voltage = 3V  $\Rightarrow$  current = 0  
and when voltage = 0, curr = -6A

Current thro' the load is ~~actually~~  $I_L$

When we are finding  $V_{Th}$ , we  
short the load and at that time  
 $I_L = 0$  so  $V_{Th} = 3V$

When we short the load, we are  
finding  $I_N$  and at that time, voltage  
across load becomes 0.

so  $I_N = 6A$

$R_N$ , Norton resistance =  $\frac{V_{Th}}{I_N} = \frac{3}{6} = 0.5\Omega$

Q2 I. For charging,

$$V_S = 40V \quad R = 5k\Omega \quad C = 10\mu F$$

Voltage attained after  $\infty$  time  $\Rightarrow 40V$

Now switch is moved so discharging

$$V_C = V_0 e^{-t/RC} \quad RC = 10 \times 10^{-6} \times 2 \times 10^3$$
$$\Rightarrow 20 \times 10^{-3}$$

$V_C$  across  $R$  at  $t = 2 \times 10^{-3} s$

$$V = 40 \times e^{-\frac{2 \times 10^{-3}}{20 \times 10^{-3}}}$$

$$40 \times e^{-\frac{1}{10}} = 36.193$$

$$I = \frac{36.193}{2 \times 10^3} \neq 10mA \quad \text{False}$$

II.  $200V = V_S \quad R = 10\Omega \quad L = 0.1H$

current at  $0.01s$

$$\tau = \frac{L}{R} = \frac{0.1}{10} = 0.01$$

So at  $t = \tau$ , current = 63.2% of initial current  $I_0$ , so current is not zero. So the statement is false

III Transient ~~or~~ disturbance is produced in the circuit when we move from one steady state to another. So this may happen when we short a circuit / change applied voltage/current source, suddenly connect / disconnect from source. So there are a lot of reasons and not just changing applied source. Hence FALSE continued after 2.4


IV. False

There are no transients in a circuit consisting of only resistance because they do not store energy unlike capacitor / resistor. They just dissipate power.

It can also happen due to faults in power system, sudden load changes, etc.

This statement is false ~~or~~ because of the usage of the word ONLY.

V.

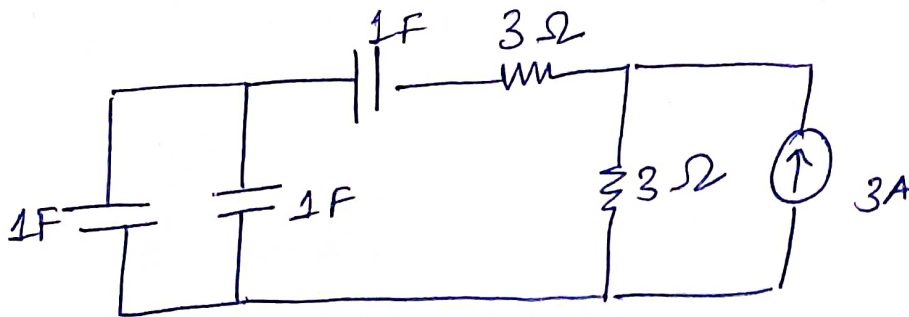


Solve in parallel

Using formula  $C_p = C_1 + C_2 \Rightarrow 2F$

Then in series w/ 1F capacitor so


$$C_{eq} = \frac{2 \times 1}{2 + 1} = \frac{2}{3} F \quad \left( C_s = \frac{C_1 C_2}{C_1 + C_2} \right)$$

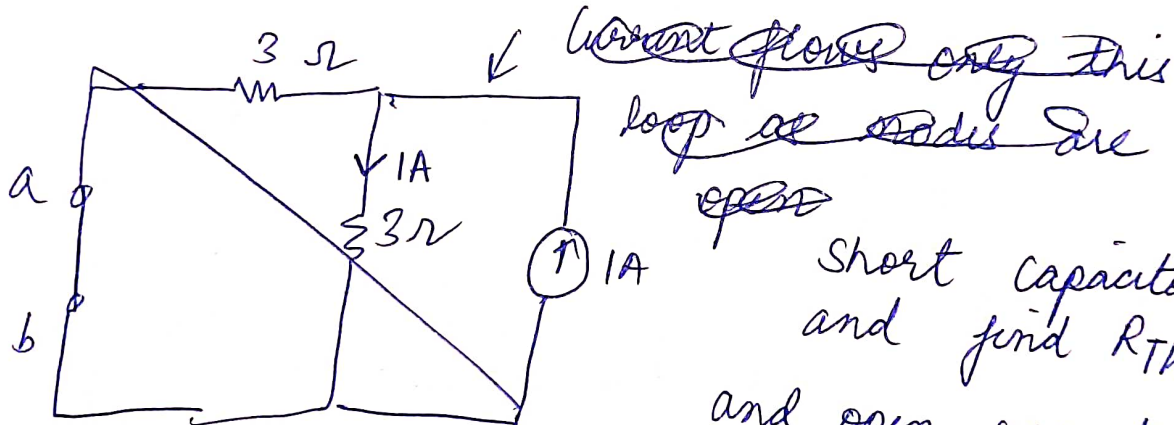Now for finding  $R_{eq}$ , we find  $R_{Th}$



Short capacitor and find  $R_{Th}$  and open current source

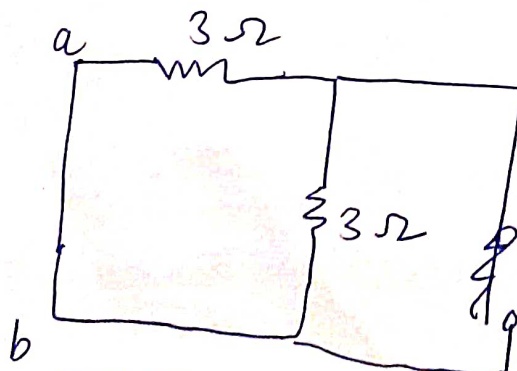So  $V_{AB} = \text{Voltage across } 3\Omega \Rightarrow 3V$



$$R_{Th} = 6\Omega$$

as  $3\Omega$  series  $3\Omega$

TRUE

So time constant

$$R_{eq} C_{eq} \Rightarrow 6 \times \frac{2}{3} = 4s$$